

# Computer Systems

## Lecture 3

# Logic Gates

**Dr José Cano, Dr Lito Michala**  
School of Computing Science  
University of Glasgow  
Spring 2020

# Outline

- Digital Circuits
- Circuit simulation
- Boolean algebra
- Making decisions: the multiplexer
- Emergent behaviour

# Lab and Quiz

- There is a weekly 2-hour lab, starting this week
- Boyd Orr 715
- Go to your scheduled lab and be sure to sit in the right section (identified as red, blue, etc.)
- There is a weekly lab sheet on Moodle, **study it in advance!**
- Each lab will have some paper and pencil problems, and some problems using the computers
- Please try the problems **before** your lab

# Hardware: Digital Circuits


- We will start with primitive components
- Study their behaviour when they are connected
- Build up a family of useful circuits
- Gradually build larger and more powerful families of circuits, using the ones already defined
- We'll end up with some circuits that can do real computing

# Logic gates

- Digital circuits are built from a very small number of primitive little machines
- Only a few are needed!
  - **Logic gates**, we'll use just four: inv, and2, or2, xor2
  - **Flip flop**, just one is needed: dff
- So we need to
  - Learn what these five components do
  - Learn how to connect them into digital circuits
 
# The Inverter

- A basic component
- Takes an input bit  $a$  and produces an output bit  $x$
- The bits are carried on **wires**
- The technical name for a wire is **signal**
- The output is the logical opposite of the input




$$x = \text{inv } a$$

a	x
0	1
1	0

# The 2-input and gate

- The output is 1 if all inputs are 1

 


$x = \text{and2 } a \ b$

a	b	x
0	0	0
0	1	0
1	0	0
1	1	1

# The 2-input inclusive or gate

- The output is 1 if any input is 1

 


$x = \text{or2 } a \ b$

a	b	x
0	0	0
0	1	1
1	0	1
1	1	1


 
# The 2-input exclusive or gate

- The output is 1 if either input is 1, but not both



$x = \text{xor2 } a \ b$

a	b	x
0	0	0
0	1	1
1	0	1
1	1	0

# Gate delay

- A logic gate is a primitive component
- It takes a small number of input bits, and produces a result according to a fixed truth table
- As long as the inputs remain stable, the output remains stable
- If an input changes at a point in time, it will take the logic gate a small amount of time to bring the output to the new value: **the gate delay**
- Gate delays are on the order of 0.01 ns (ns = nanosecond, there are  $10^9$  ns per second)
- May be faster or slower, depending on the technology

# Combinational circuits

- A combinational circuit...
  - Consists of logic gates connected together
  - The circuit has some inputs and produces some outputs
  - It contains no feedback loops
  - The outputs depend on the current input values (i.e. the circuit has no memory)


# Outline

- Digital Circuits
- Circuit simulation
- Boolean algebra
- Making decisions: the multiplexer
- Emergent behaviour

# Circuit simulation


- When you learn to program, you learn how to “execute a program by hand”
- This is an essential skill
  - It helps to understand how the computer executes the program
  - It enables you to understand bugs
- For a digital circuit, the equivalent skill is **circuit simulation**
  - You're given the inputs to a circuit
  - You calculate what its outputs should be, by doing the same calculations the hardware would make

# Connecting components with wires

 


 
# An integrated circuit: Intel A80186 CPU




# How to simulate a combinational circuit

- You're given the inputs to the circuit
  - The other signal values are unknown
- Find an output of a logic gate where all the inputs are known, and write down the output value
  - Using the truth table for the logic gate
- Repeat until all signals are known


 
# Example of circuit simulation


- Inputs are a, b, c (each is a bit)
- Output is x (a bit)



- Given specific values of a, b, c, what is the output x?

 
# Example of circuit simulation

- First, we're given the inputs to the circuit
- Other signals are unknown


 
# After one gate delay


- Look for a component where all the inputs are known, and note the value of its output sigma



- In this example, we can't simulate the or2 gate, because we don't yet know its top input
  - But we can simulate the and2 gate, and its output is 0
 
## After two gate delays

- Look for a component where all the inputs are known, and note the value of its output signal



- Continue the process until all signals are known

# Outline

- Digital Circuits
- Circuit simulation
- **Boolean algebra**
- Making decisions: the multiplexer
- Emergent behaviour

# Introduction to Boolean algebra

- **Boolean algebra** is a good notation for logic gates
  - There are two values: 0, 1
  - We can use variables to stand for a value: x, y, z, ...
  - There are three operators
  - Each operator corresponds exactly to a logic gate
  - Boolean algebra **describes the values of signals in a digital circuit**

Algebra	Name	Circuit
$\neg x$	not	inv x
$x \vee y$	or	or2 x y
$x \wedge y$	and	and2 x y

# Laws of Boolean algebra

- Ordinary algebra has laws that you can use to simplify expressions, examples:

$$- x + y = y + x$$

$$- x + 0 = x$$

- Boolean algebra does too! Here are a few of them:

$$x \wedge 0 = 0$$

$$x \wedge 1 = x$$

$$x \vee 0 = x$$

$$x \vee 1 = 1$$

- These are very important, and we will shortly use them to calculate how a circuit works

# Building block circuits

- To do “useful stuff” a circuit usually needs to be fairly big
- But it's hard to understand or to design a really big circuit
- The solution is **abstraction**
  - We will put several components together to build a **black box circuit**
  - Then several of those will combine to make a bigger one
  - And then a still-larger one...
- We're going to look at several example circuits that are **really important**
  - They are critically important in computers




# Outline

- Digital Circuits
- Circuit simulation
- Boolean algebra
- Making decisions: the multiplexer
- Emergent behaviour
 
# Multiplexer

- The **multiplexer** is the fundamental circuit used to **make decisions**
- A multiplexer is a hardware version of the if-then-else expression
- The idea is to choose between two values (x, y) based on another value (c)
  - Given three inputs: c, x, y
  - Produces one output
    - If  $c = 0$  the output is x
    - If  $c = 1$  the output is y
- In digital hardware circuits, there are no statements
  - So, there are no “if statements” to determine whether other statements should be executed
  - Instead, we have signals whose values depend on other signals

Multiplexer:  $z = (\text{if } c=0 \text{ then } x \text{ else } y)$




# Simulating the multiplexer

To find out what the circuit does, simulate it!


- Given a set of input values, you can calculate the corresponding output
- **Example:** Suppose  $c = 1$ ;  $x = 0$ ;  $y = 1$ 
  - The inverter outputs 0, the first and gate has inputs 0 and 0 so it outputs 0
  - The second and gate has inputs 1 and 1 so it outputs 1
  - The or2 gate has inputs 0 and 1 so it outputs 1, which is the output of the entire circuit
- By doing this for all 8 sets of input values, you can fill in the truth table for the circuit, which fully describes its behaviour
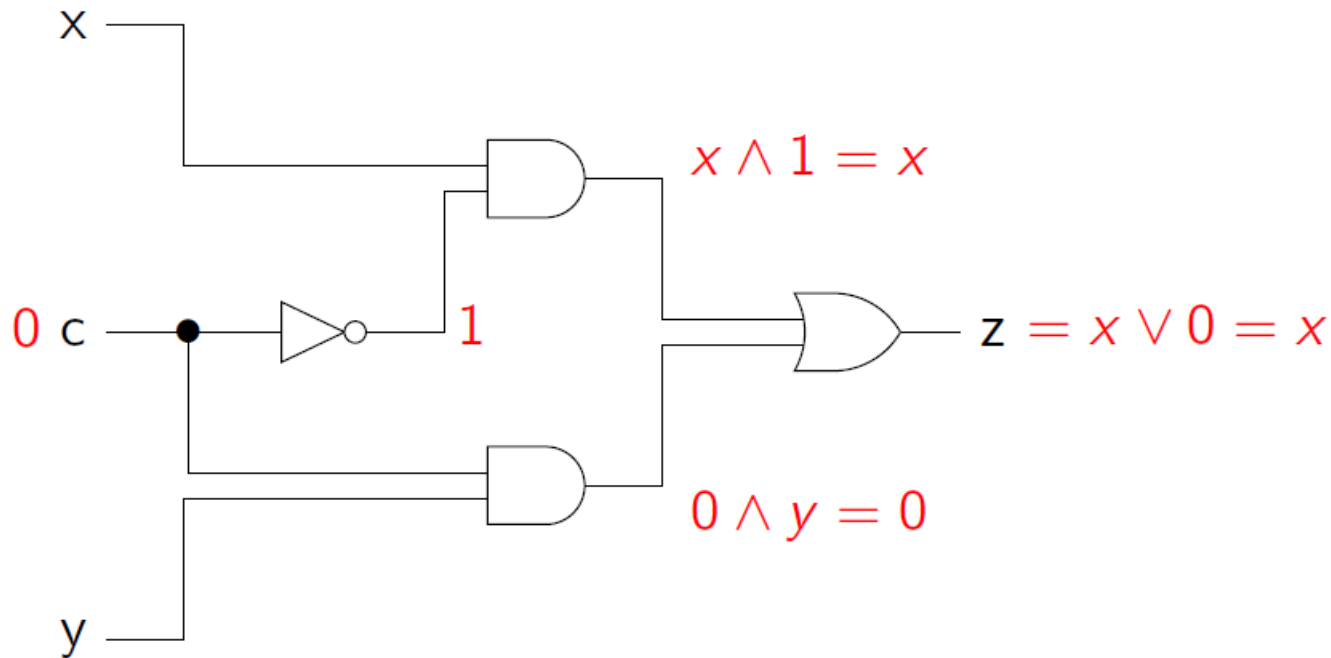
# Multiplexer when $c=0$ : $z = (\text{if } c=0 \text{ then } x \text{ else } y) = x$

- We can calculate the output  $z$  using Boolean algebra



 Multiplexer when  $c=1$ :  $z = (\text{if } c=0 \text{ then } x \text{ else } y) = y$



# Truth table for mux1

c	x	y	out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Meaning of the multiplexer

- $\text{mux1 } c \ x \ y = \text{if } c \text{ is zero then } x \text{ else } y$

c	x	y	out
0	<b>0</b>	0	<b>0</b>
0	<b>0</b>	1	<b>0</b>
0	<b>1</b>	0	<b>1</b>
0	<b>1</b>	1	<b>1</b>
1	0	<b>0</b>	<b>0</b>
1	0	<b>1</b>	<b>1</b>
1	1	<b>0</b>	<b>0</b>
1	1	<b>1</b>	<b>1</b>



# Multiplexers are important!

- Multiplexers are a central black box which we will use again and again
- One way to understand the circuit is to calculate its truth table by simulating it for each set of input values
- Most conditional operations in digital circuits are implemented, at the lowest level, by a multiplexer
- In a circuit, we don't "execute if-then-else statements", there are no statements!
  - Instead, we define signals using if-then-else expressions, implemented with multiplexers

# Outline

- Digital Circuits
- Circuit simulation
- Boolean algebra
- Making decisions: the multiplexer
- Emergent behaviour

# Emergent behaviour

- Some systems have these characteristics
  - They comprise parts with relatively simple behaviour
  - The whole system has complicated behaviour
  - This complex behaviour **emerges** from the interaction of the simple parts
- Examples in science, sociology, politics, philosophy, ...

# Complex computing from simple logic gates

- Each of our five primitive devices has **extremely simple behaviour**
- You can understand completely what each of them does
- None of them does anything remotely like computing
  - They can't do arithmetic
  - They can't execute statements
  - They can't make decisions
  - They can't do much at all!
- So how can a computer work?
  - All the interesting things that a computer can do are **emergent behaviours**
  - Emergent means that a system whose components are all simple can exhibit complex behaviour

# Examples of emergent behaviour


- **Chemistry:** The ideal gas law
- **Biology:** Motion of a flock of birds
- **Computing:** Addition of binary numbers

# Decisions

- Ultimately, all decisions become a choice of two alternative values on a signal (wire)
- All of these choices are made by the multiplexer circuit
  - Its behaviour is clearly conditional: the output is  $x$  if  $c = 0$ , otherwise it's  $y$
  - Yet the implementation of the multiplexer just uses a few logic gates
- This is the fundamental point where conditional behaviour emerges from a lower level behaviour of logic gates!
- Every decision that a computer system makes ultimately comes down to a multiplexer!
 
# To do

- Revise the lecture slides
- Solve the tutorial exercises (they are on Moodle)
- Check MyCampys->My Student Centre->My Calendar to find your Lab Group.
  - Remember that attendance will be taken at the lab
  - It is your responsibility to find your Tutor
- Go to the lab and discuss the exercises
- Ask questions about any of the lecture material



<https://xkcd.com/571/>