

Computer Systems

Lecture 6

Register Transfer Machine

Dr José Cano, Dr Lito Michala

School of Computing Science

University of Glasgow

Spring 2020

Outline

- Calculators and memory
- Register File
 - Behaviour of register File
 - Loading: the demultiplexer
 - Readout: the multiplexer
 - Register file circuit
- Arithmetic: the adder
- Register Transfer Machine

Assignment statements and circuits

- A program uses assignment statements to calculate results

$x := 2 + 2$

$y := 3 * (x + 1)$

- **Our goal:** a digital circuit that can do this!

Instructions

- The expression in the right hand side of an assignment statement can be arbitrarily large and complex
- For a digital circuit, we need
 - Simple statements (e.g. just one arithmetic operation)
 - Statements with a fixed form
 - A small number of types of statement
- These are called instructions
- Our circuit will use two instructions, of the form
 - $R2 := 6$
 - $R3 := R1 + R0$

Outline

- Calculators and memory
- Register File
 - Behaviour of register File
 - Loading: the demultiplexer
 - Readout: the multiplexer
 - Register file circuit
- Arithmetic: the adder
- Register Transfer Machine

Register file

- A register file is an array of registers: R0, R1, R2, R3, etc
- Each variable is held in a register
- We refer to a variable by its address
 - An address is a binary number 0, 1, 2, 3, ...
- What the register file circuit does
 - Contains the array of registers
 - Each register holds a word (a binary number)
 - Enables to specify an address and read out that register
 - Enables to specify another address and load a data value into that register


Behaviour of register file

- The behaviour is
 - At clock tick: $\text{if } ld = 1 \text{ then } Reg[d] := x$
 - During clock cycle: $a = Reg[sa] \text{ and } b = Reg[sb]$
- The operation is determined by the control signals ld , d , sa , sb
- The data input is x , and there are two data outputs a , b


Loading into a register file: demultiplexer

- Often, every register in the register file retains its previous state
- Sometimes we will modify one (just one!) register in the register file
- We need a way to take a destination register number (R0 or R1) and tell just that register to perform a load
- This is done with a demultiplexer
- R0 and R1 each need an individual load control
- The register selected by d gets the register file *load* input
- The register not selected by d gets a load control of 0


demux1: generate 2 control signals from a bit address

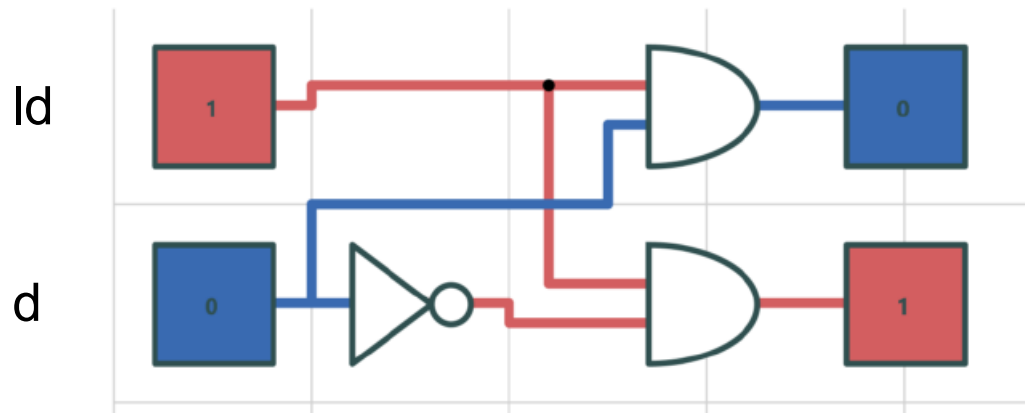

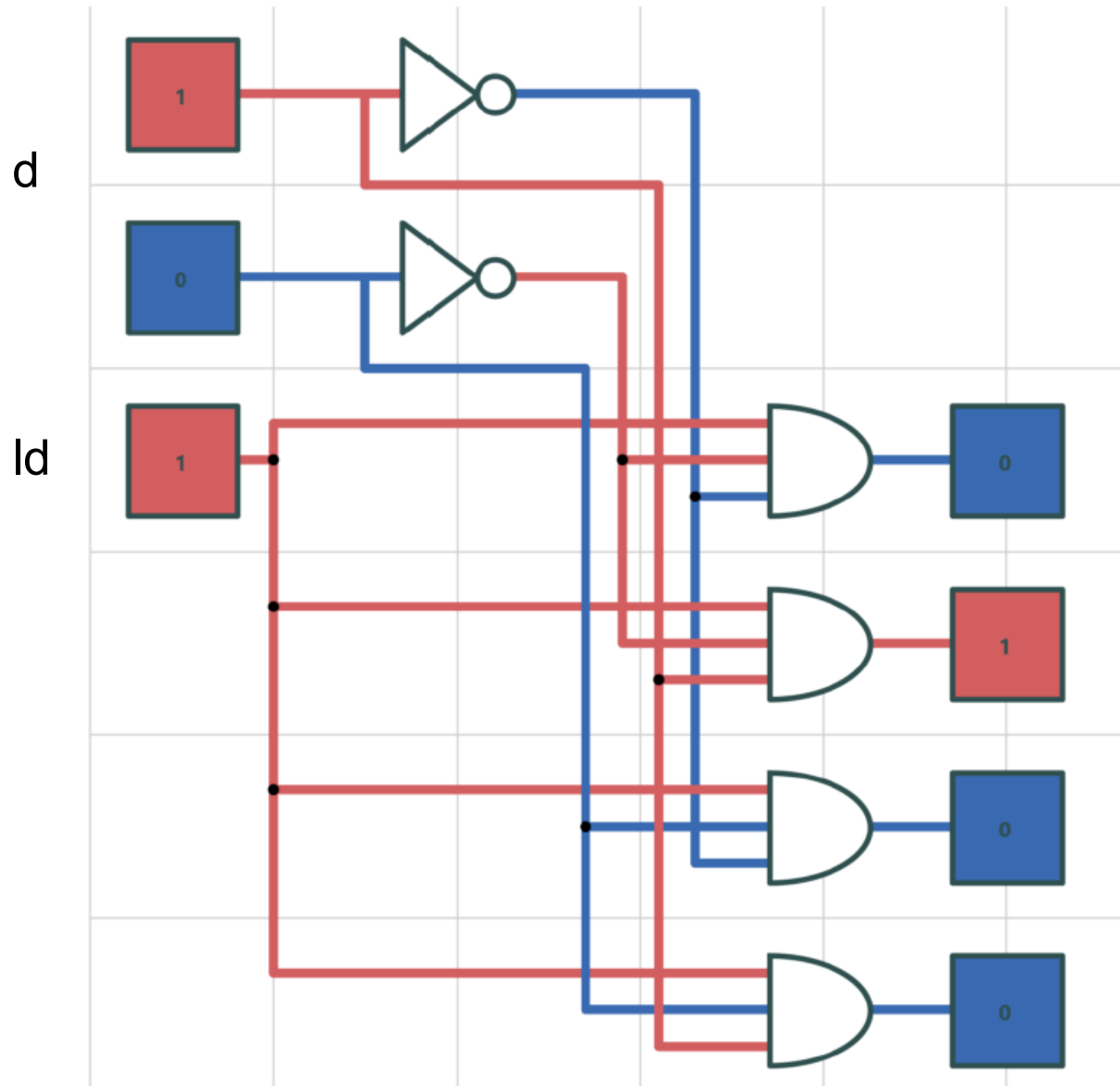demux2: generate 4 control signals from 2-bit address



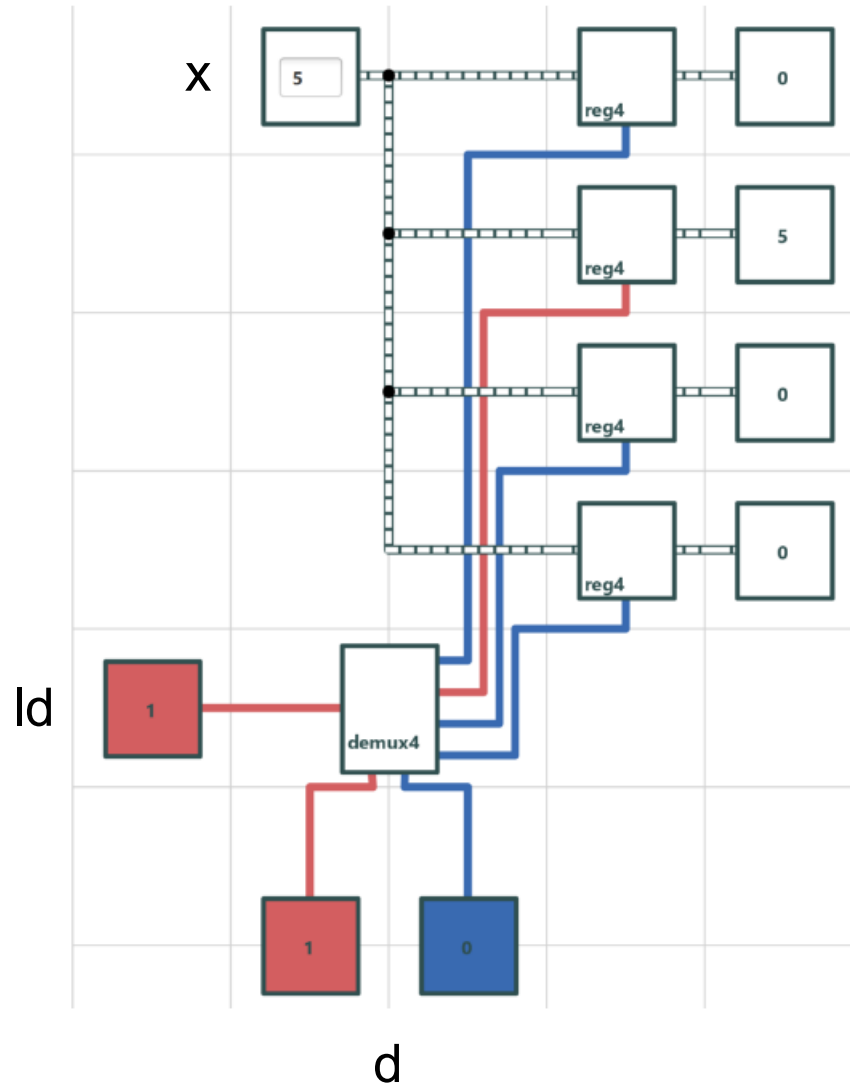
Register file with demultiplexers: $R2 := x$




Multiplexers

- A bit-level multiplexer `mux1` uses a `control bit` to choose between `two data bits`
- The word-level multiplexer `wmux1` uses a `control bit` to choose between `two data words`
- A multiplexer for 4-bit words consists of 4 copies of the basic multiplexer

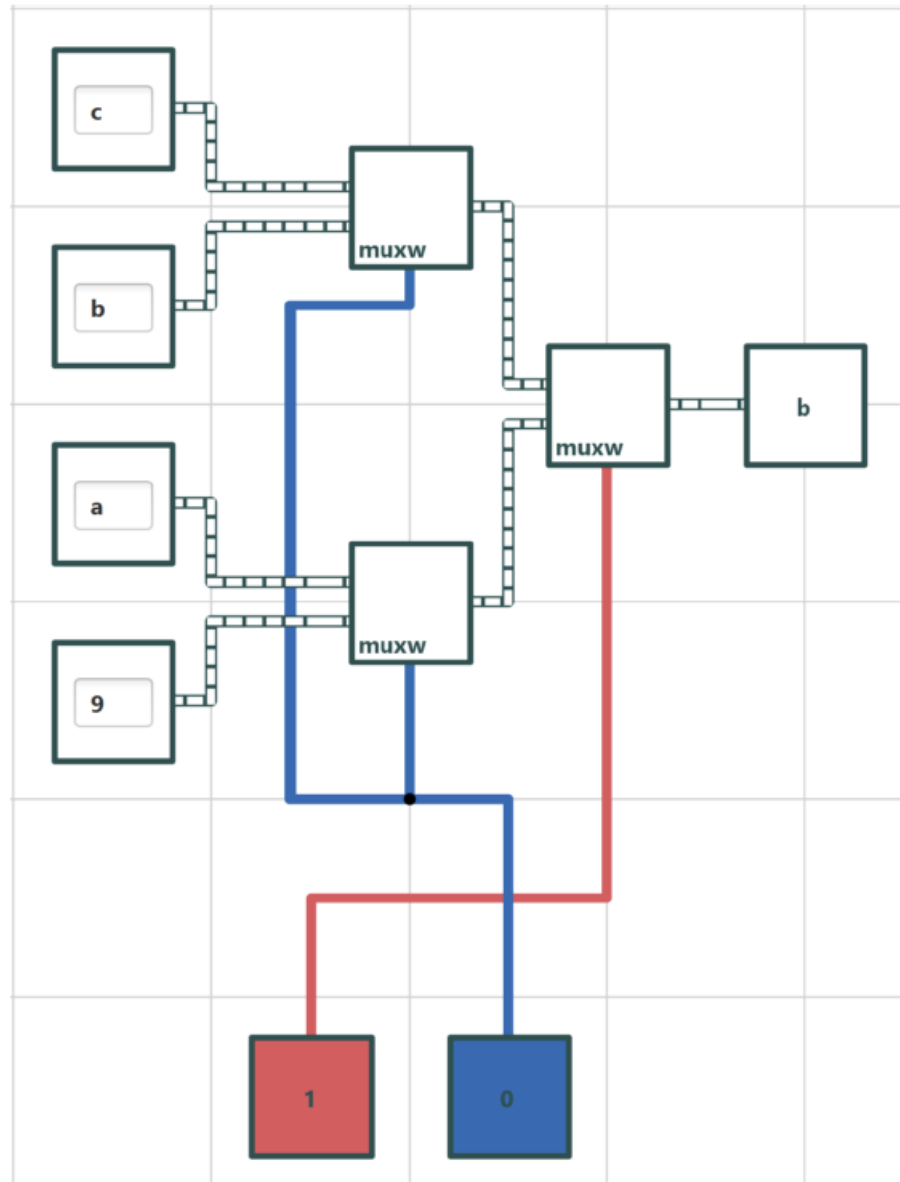
mux2w: choose among 4 values with 2-bit address



Multiplexers: readout R1

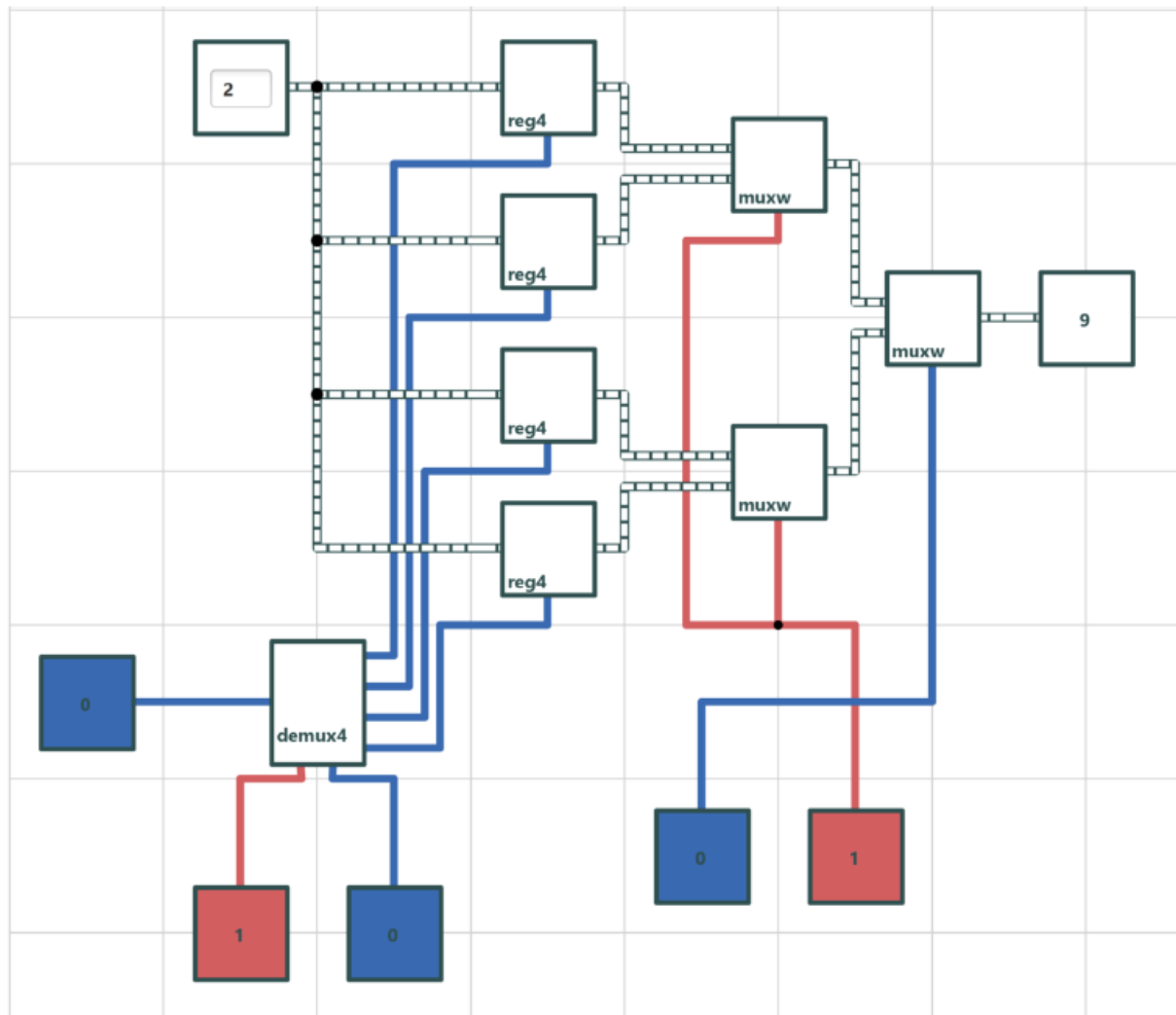

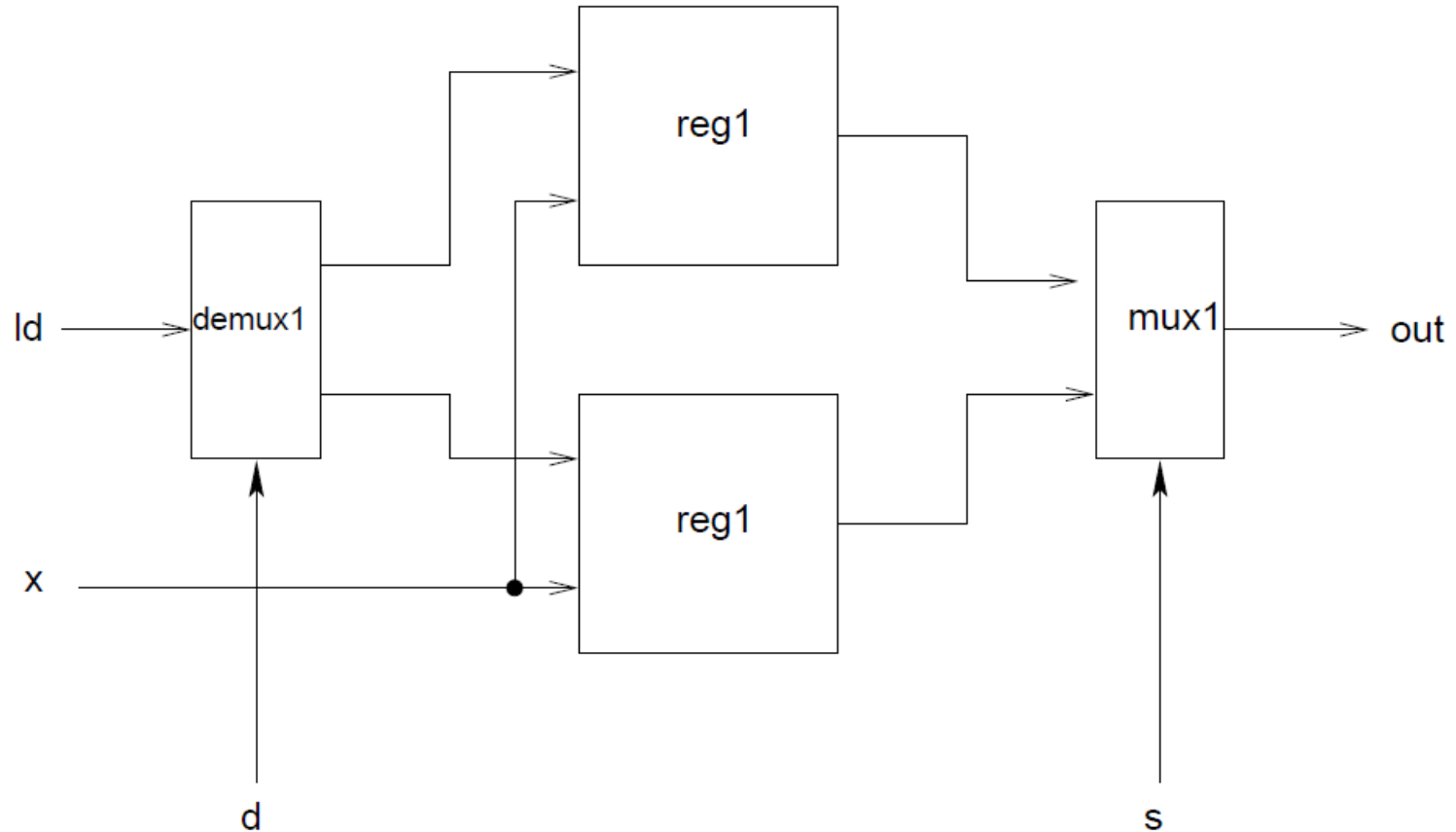Simple register file: 2 registers, 1 readout




The output is the value of $reg[s]$ - At a clock tick, if `ld` then $reg[d] := x$

Register File with 2 readouts

- Our aim is to do calculations like $p + q$ or $x - y$
- The variables will be in registers
- So we need to read out two registers, not just one
- Therefore we extend the register file so we give it two source addresses sa , sb and it will read out both
 - $a = \text{reg}[sa]$
 - $b = \text{reg}[sb]$


Register File with 2 readouts

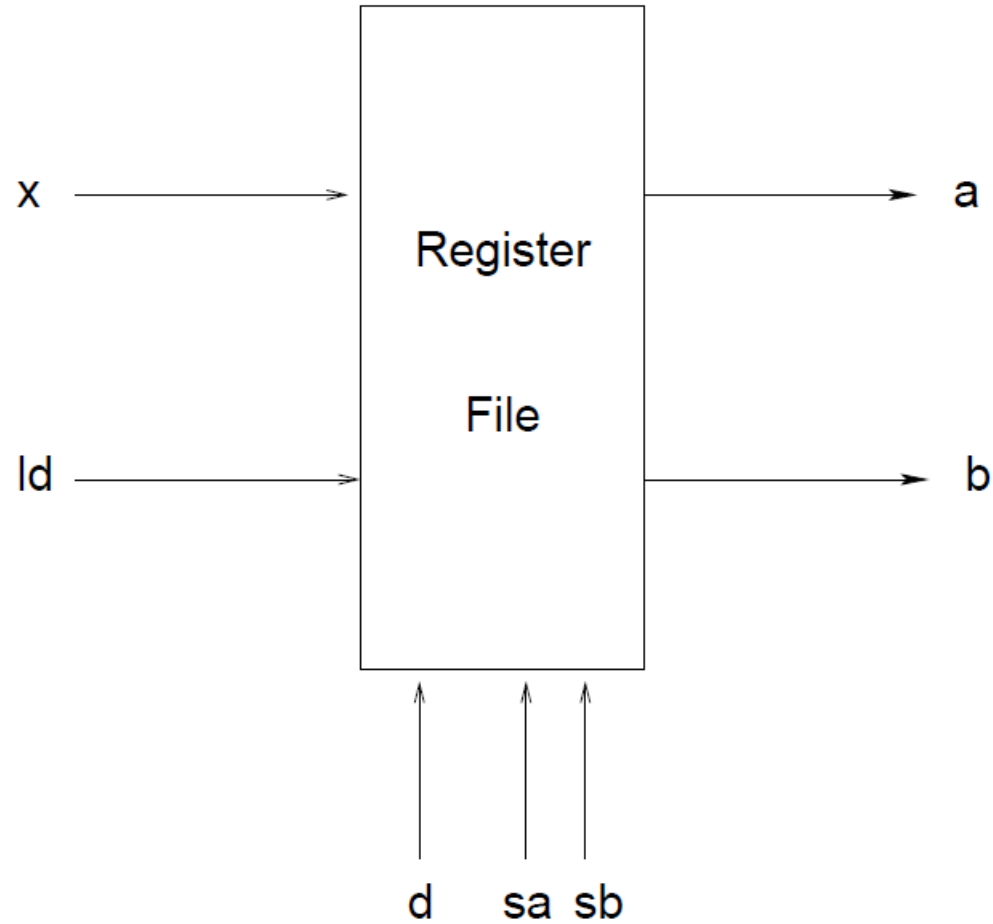

Outline

- Calculators and memory
- Register File
 - Behaviour of register File
 - Loading: the demultiplexer
 - Readout: the multiplexer
 - Register file circuit
- Arithmetic: the adder
- Register Transfer Machine

add4: $6 + 7 = d$

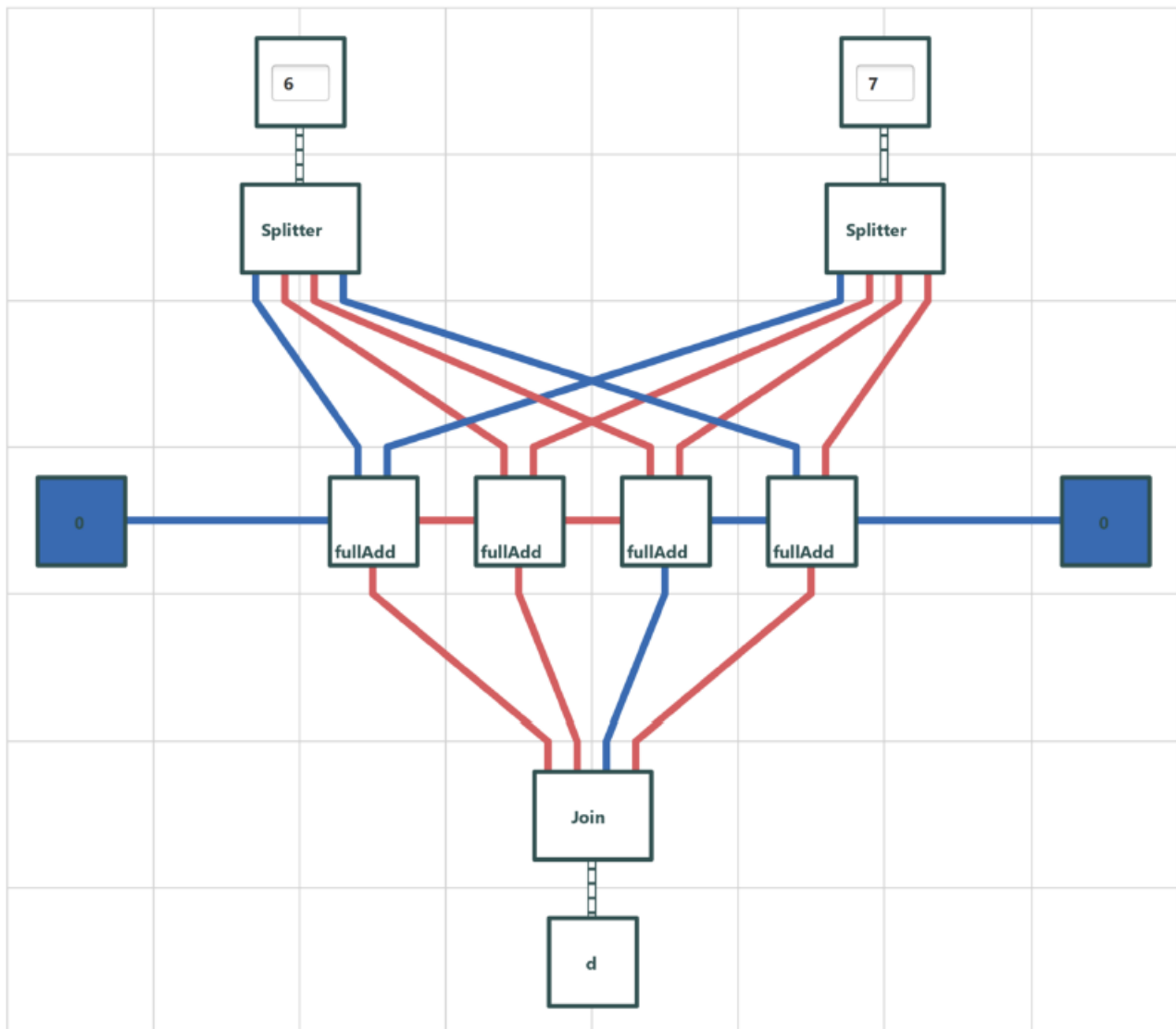


Outline

- Calculators and memory
- Register File
 - Behaviour of register File
 - Loading: the demultiplexer
 - Readout: the multiplexer
 - Register file circuit
- Arithmetic: the adder
- Register Transfer Machine

Register Transfer Machine (RTM)

- The register file produces two outputs and the adder requires two inputs
- The adder produces one data word output, and the register file takes one data word input
- We can connect them in a feedback loop!
- The effect will be (at a clock tick)
 - *if ld then $reg[d] := reg[sa] + reg[sb]$*
- Add an external data input, and use a multiplexor to decide whether the external input or the ALU result should be sent to the register file

Register Transfer Machine: Circuit

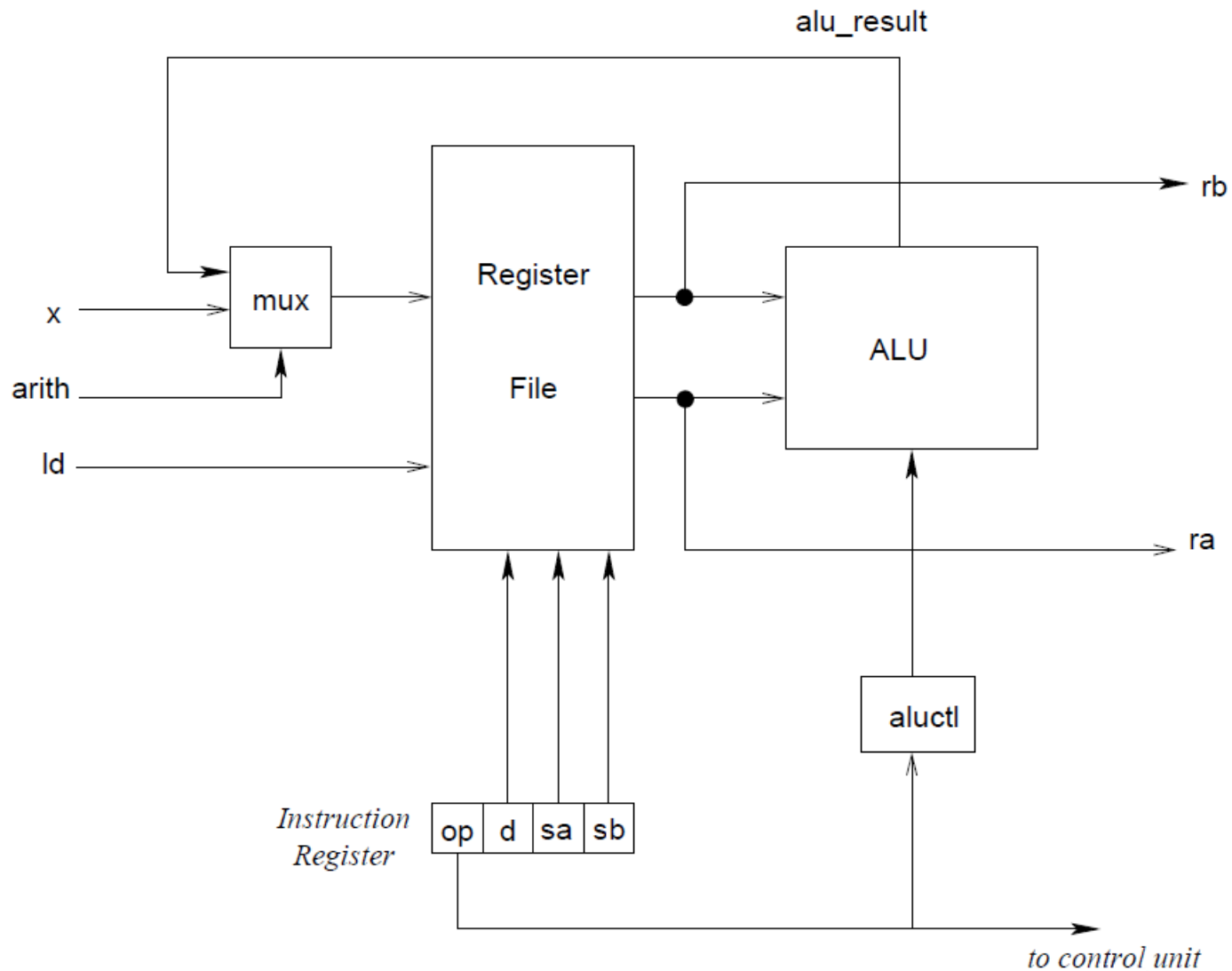

Behaviour of RTM

- Data input x
- Control inputs ld , $arith$
- Address inputs d , sa , sb (specify registers)

- At clock tick

if ld


then if $arith$

then $reg[d] := reg[sa] + reg[sb]$


else $reg[d] := x$

- All other registers remain unchanged (the variables you aren't assigning to don't change)

RTM: $R3 := 7$

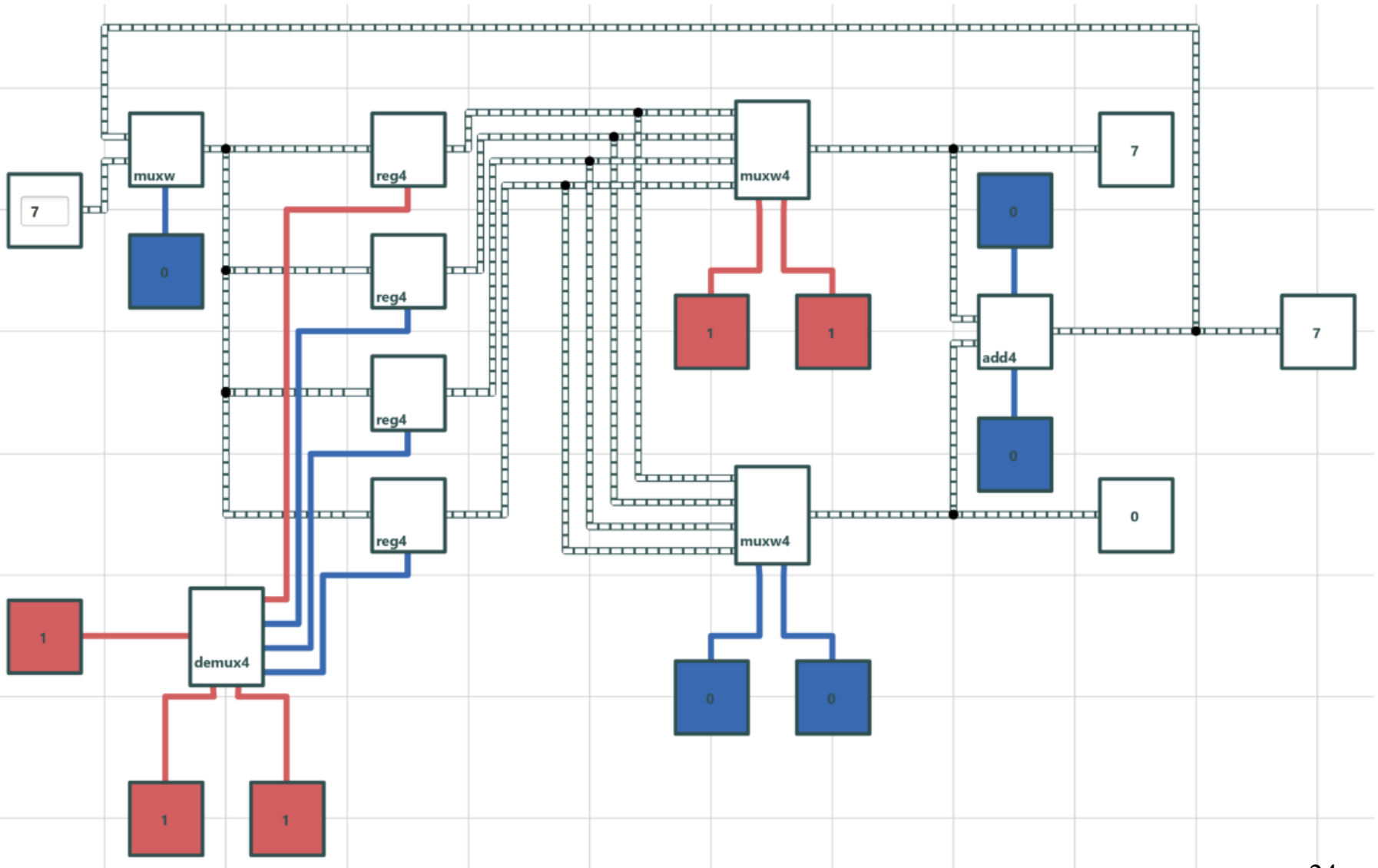

RTM: $R3 := 7; R2 := 5; R1 := R3 + R2$

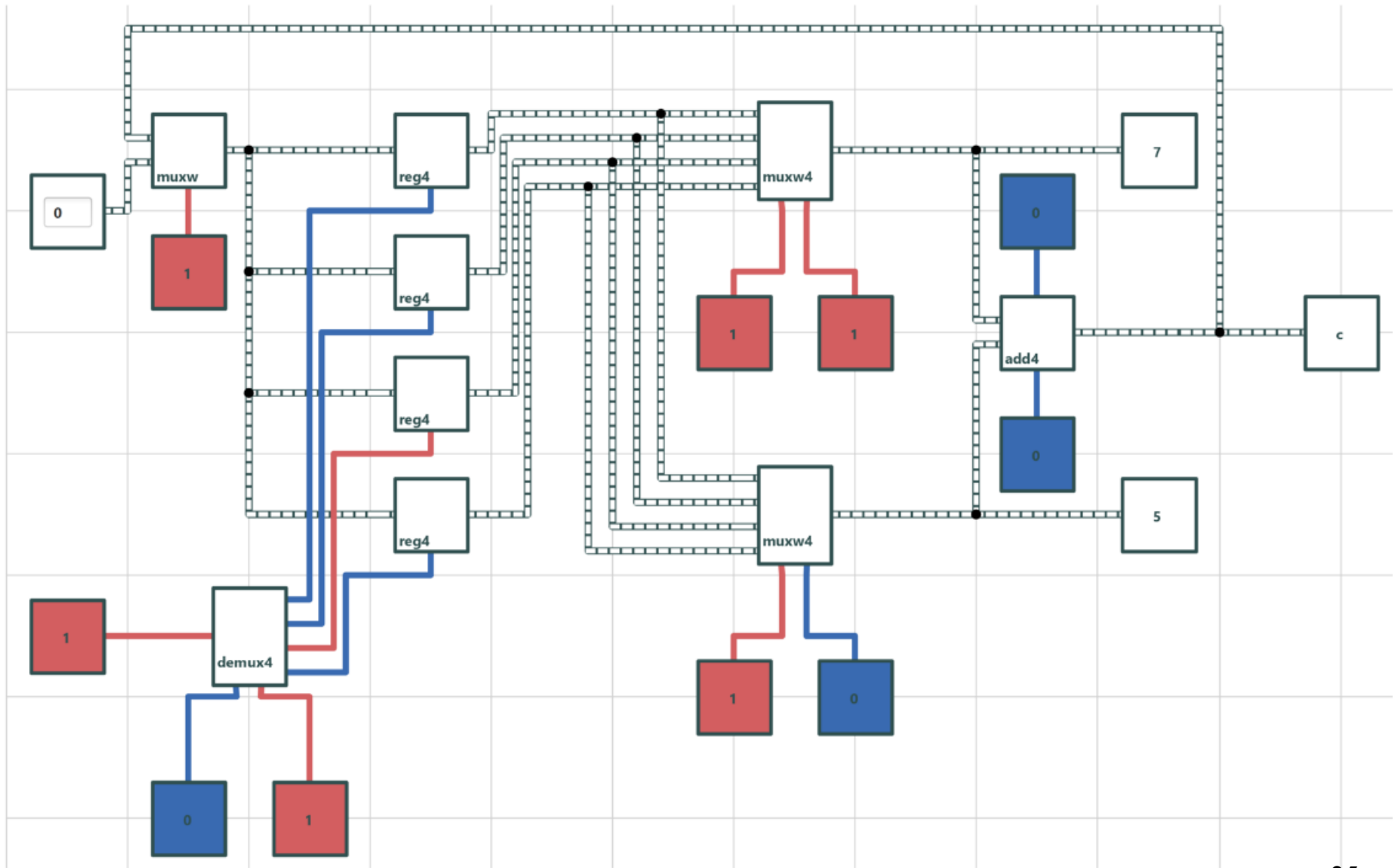

Register Transfer Machine in Logic Works

- We have simplified the description of the circuit using 4-bit components and 4-bit signals
- But in the real hardware, all of the logic gates and wires are really there
- Real circuits are complicated!



Controlling a circuit

- The “core” of the circuit is a register file and an adder
- To make it perform useful computations, we need to control it
- This is done with control signals
- A control signal is a bit (either 0 or 1), just like any other signal
- But it helps conceptually to make a distinction between data signals and control signals

An analogy: Marionnette

- There are lots of systems with
 - A core part that does something
 - An external operator that tells the core what to do
 - Control signals that enable the operator to control the core
- A traditional example: the Marionnette
 - A doll that can move around, like an actor
 - A person (out of sight) manipulating the doll
 - Strings the person can pull, controlling the doll
- This is the origin of the expression “to pull strings” or “to pull someone's strings”
- See one in action:
 - <https://www.youtube.com/watch?v=SPBm8I7hoBQ>

Marionette: controlled by pulling strings



- By SoHome Jacaranda Lilau, Tamelifa Puppeters, Pierre S Frana Line - Own work, CC BY-SA 3.0 <https://commons.wikimedia.org/w/index.php?curid=8392787>

Running a simple program on RTM

- For now, let's just consider a fixed sequence of simple assignment statements
- Each variable must be a register: R0, R1, R2, R3
- Each statement must be written in one of these forms
 - $\text{reg} = \text{constant}$
 - $\text{reg} = \text{reg} + \text{reg}$
 - $\text{reg} = \text{reg} - \text{reg}$
- Example:
 - $R1 = 3$
 - $R2 = 1$
 - $R3 = R1 + R2$
 - $R1 = R2 - R2$
- We can execute this program on the RTM!

What can you make the circuit do?

- You'll operate the circuit so that it will execute little programs like this

$R0 := 4$; $R0 = 4$

$R1 := 6$; $R1 = 6$

$R2 := R0 + R1$; $R2 = a$

$R0 := R0 + R2$; $R0 = e$

$R3 := 1$; $R3 = 1$

$R1 := R1 + R1$; $R1 = c$

How to execute $R1 := 5$

- Tell it to use the indata input (the hex keypad) as the data input to register
file: `ctl_add = 0`
- Tell it to put the data into R1: `ctl_d1, ctl_d0 = 01`
- Tell it to perform a load
 - Actually, the circuit does a load every clock cycle, but in a real computer we would have to set `ctl_ld = 1`
- **Note:** the values of `ctl_sa1`, `ctl_sa0`, `ctl_sb1`, `ctl_sb0` don't matter
 - The registers they specify will be read out and you can look at them on the hex displays, but these values won't actually be used
- Perform a clock tick: pulse clock (click it to 1, then click it to 0)

How to execute $R2 := R0 + R3$

- Tell it to read out R0 on the a output: `ctl_sa1, ctl_sa0 = 00`
- Tell it to read out R3 on the b output: `ctl_sb1, ctl_sb0 = 11`
- Tell it to use the adder output as the data input to register file: `ctl_add = 1`
- Tell it to put the data into R2: `ctl_d1, ctl_d0 = 10`
- Tell it to perform a load
 - Actually, the circuit does a load every clock cycle, but in a real computer we would have to set `ctl_ld = 1`
- Note: the value of `indata` is ignored, so you can set it to any value you like, makes no difference
 - This is called a “don't care” value
- Perform a clock tick: pulse clock (click it to 1, then click it to 0)

Beyond the RTM

- The RTM can execute a simple sequence of assignments
- We can extend it gradually to turn it into a computer
 - Enable it to subtract as well as add
 - Provide a way to set the control signals automatically, not by hand
 - Give it the ability to make decisions (if-then-else)
- We won't add all these capabilities to the circuit, but will look at the end result

To do

- Be sure to complete last week's quiz
- This week's quiz will be available after lecture
- Study the key circuits: register file and register transfer machine
- You don't need to memorise the circuits
- Just understand the general ideas



<https://xkcd.com/722/>